

Please check that this question paper contains 09 questions and 02 printed pages within first ten

[Total No. of Questions: 09]

[Total No. of Pages: ..02....]

Uni. Roll No.

Program: B.Tech. (Batch 2018 onward)

Semester: 4th

Name of Subject: Digital Electronics

Subject Code: PCEE-105

Paper ID: 16186

Time Allowed: 03 Hours

Max. Marks: 60

NOTE:

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

Part – A

[Marks: 02 each]

Q1.

- a) Convert $(B7.9AD)_{16} = (?)_2 = (?)_{10}$
- b) Solve the expression using Boolean law $Y = ABC\bar{C} + (A + B)(\bar{A} + B)$
- c) Write an expression of maximum frequency of operation of n bit Asynchronous and synchronous counters.
- d) Give advantages of R2R ladder type DAC over Weighted resistor type DAC.
- e) Comparison SRAM and DRAM.
- f) Design logic circuit for 3 line to 8 line decoder.

Part – B

[Marks: 04 each]

- Q2.** Formulate AND Gate, OR Gate, NOT Gate and NOR Gate using NAND gates.
- Q3.** Design the circuit for Full Adder with the help of Logic Gates. Give applications
- Q4.** What is multiplexer? Obtain an 8:1 multiplexer using two 4:1 multiplexer.
- Q5.** Draw 3-bit down counters. Explain its working with the help of truth table.
- Q6.** Comment on the parameter which serve to describe the quality of performance of D/A converters.
- Q7.** Explain the construction and operation CCD memory and its advantages.

Part – C

[Marks: 12 each]

- Q8. A four variable function is given as $F = \sum m(0, 2, 4, 8, 9, 10, 14) + d(1, 7, 13, 15)$.
- Express in Canonical POS form
 - Express in Canonical SOP form
 - Find the minimized Boolean expression using K maps and realized it using NOR gates only.

or

Describe in detail master slave JK Flip Flop with the help neat waveforms and truth table.

- Q9. a. What is PAL? Explain.
b. Show how PAL is programmed for the following logic function.

$$X = AB'C + A'BC' + A'B' + AC$$

or

Describe the working of successive approximation A/D converter with the help of suitable diagram and compare its performance in terms of speed, accuracy and resolution.
